

**SRI SHANMUGHA COLLEGE OF ENGINEERING AND
TECHNOLOGY**

**DEPARTMENT OF ELECTRONICS AND COMMUNICATION
ENGINEERING**

LAB MANUAL

EC8661-VLSI DESIGN LAB

REGULATION 2017

| EX. NO | DATE | NAME OF THE EXPERIMENT | MARK | SIGNATURE |
|--------|------|------------------------|------|-----------|
| 1 | | | | |
| 2 | | | | |
| 3 | | | | |
| 4 | | | | |
| 5 | | | | |
| 6 | | | | |
| 7 | | | | |
| 8 | | | | |
| 9 | | | | |
| 10 | | | | |
| 11 | | | | |
| 12 | | | | |

LIST OF EXPERIMENTS:**Part I: Digital System Design using HDL & FPGA (24 Periods)**

1. Design an Adder (Min 8 Bit) using HDL. Simulate it using Xilinx/Altera Software and implement by Xilinx/Altera FPGA
2. Design a Multiplier (4 Bit Min) using HDL. Simulate it using Xilinx/Altera Software and implement by Xilinx/Altera FPGA
3. Design an ALU using HDL. Simulate it using Xilinx/Altera Software and implement by Xilinx/Altera FPGA
4. Design a Universal Shift Register using HDL. Simulate it using Xilinx/Altera Software and implement by Xilinx/Altera FPGA
5. Design Finite State Machine (Moore/Mealy) using HDL. Simulate it using Xilinx/Altera Software and implement by Xilinx/Altera FPGA
6. Design Memories using HDL. Simulate it using Xilinx/Altera Software and implement by Xilinx/Altera FPGA

Part-II Digital Circuit Design (24 Periods)

7. Design and simulate a CMOS inverter using digital flow
8. Design and simulate a CMOS Basic Gates & Flip-Flops
9. Design and simulate a 4-bit synchronous counter using a Flip-Flops
Manual/Automatic Layout Generation and Post Layout Extraction for experiments 7 to 9
Analyze the power, area and timing for experiments 7 to 9 by performing Pre Layout and Post Layout Simulations.


Part-III Analog Circuit Design (12 Periods)

10. Design and Simulate a CMOS Inverting Amplifier.
11. Design and Simulate basic Common Source, Common Gate and Common Drain Amplifiers.
Analyze the input impedance, output impedance, gain and bandwidth for experiments 10 and 11 by performing Schematic Simulations.
Design and simulate simple 5 transistor differential amplifier. Analyze Gain,
12. Bandwidth and CMRR by performing Schematic Simulations.


CONTENT BEYOND SYLLABUS:

1. Design and Simulate a Ripple Carry Adder
2. Design and Simulate a Multiplexer and De-Multiplexer.

VLSI DESIGN

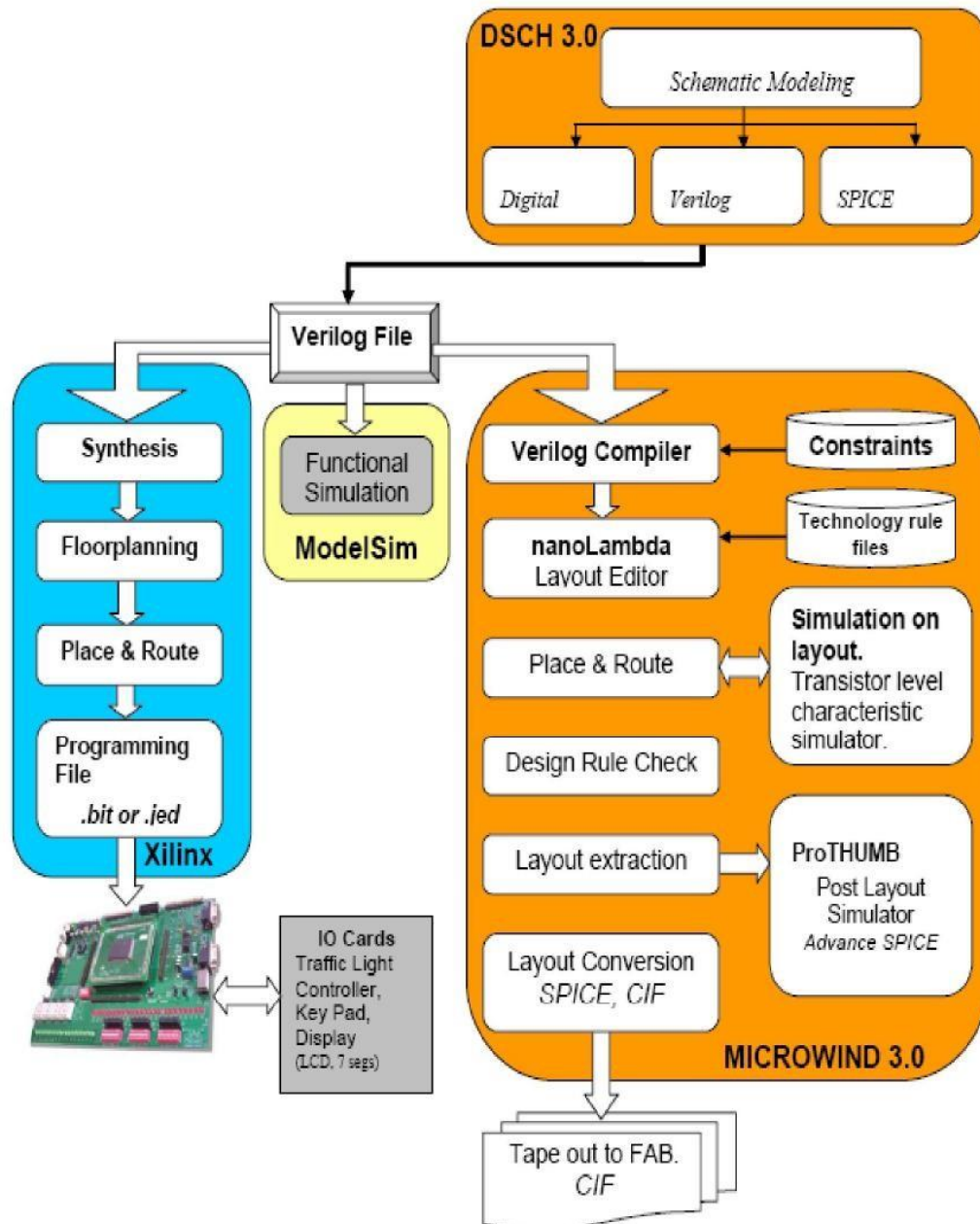

ASIC DESIGN FLOW

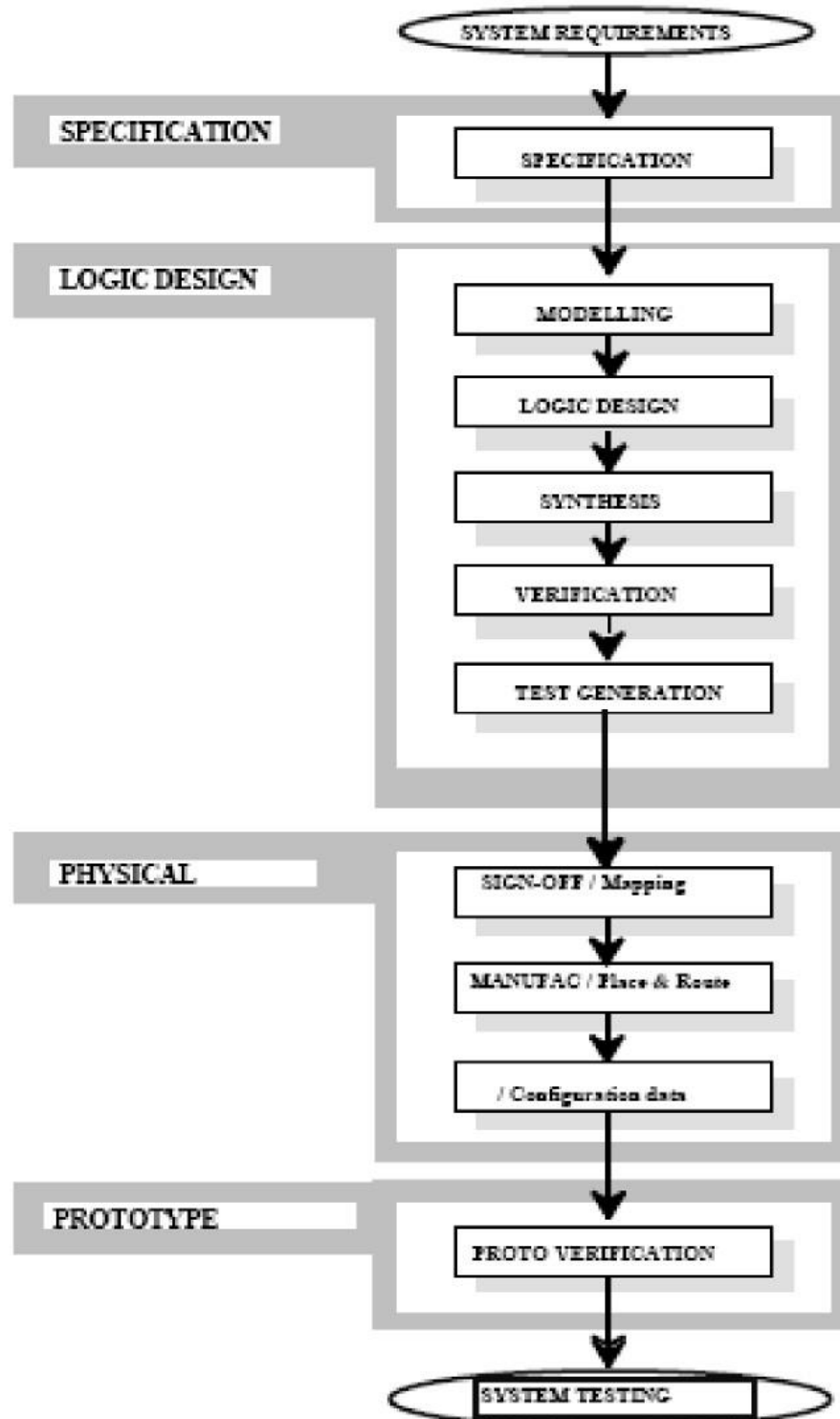

Design of Logic gates

1.1 Introduction

The purpose of this experiment is to simulate the behavior of several of the basic logic gates and you will connect several logic gates together to create simple digital model.

12 Software tools Requirement

Equipments:

Computer with Modelsim Software

Specifications:

HP Computer P4 Processor - 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Softwares: Modelsim - 5.7c, Xilinx - 6.1i.

Algorithm

STEP 1: Open ModelSim XE II / Starter 5.7C

STEP 2: File -> Change directory -> D:\<register number>

STEP 3: File -> New Library -> ok

STEP 4: File -> New Source -> Verilog

STEP 5: Type the program

STEP 6: File -> Save -><filename.v>

STEP 7: Compile the program

STEP 8: Simulate -> expand work -> select file -> ok











STEP 9: View -> Signals



STEP 10: Select values -> Edit -> Force -> input values

STEP 11: Add -> Wave -> Selected signals -> Run

STEP 12: Change input values and run again

13 Logic Gates and their Properties
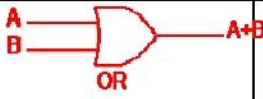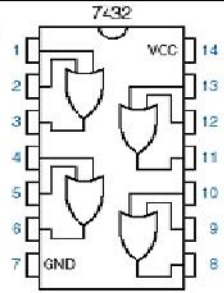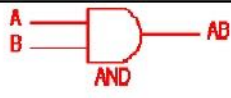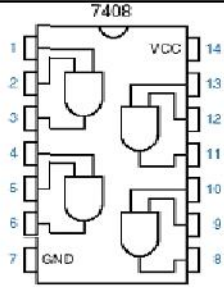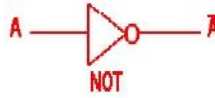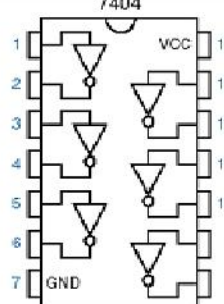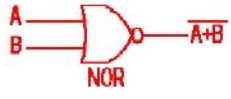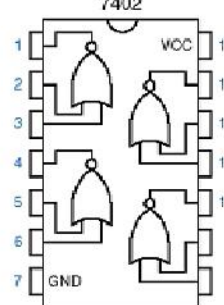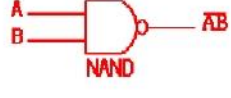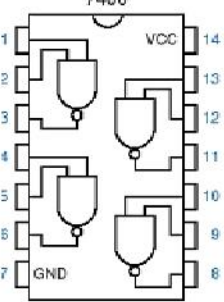
| Gate | Description | Truth Table | | | Logic Symbol | Pin Diagram |
|------|--|-------------|---|----------|--|---|
| OR | <p>The output is active high if any one of the input is in active high state, Mathematically,</p> <p>$Q = A+B$</p> | A | B | Output Q |  |  |
| AND | <p>The output is active high only if both the inputs are in active high state, Mathematically,</p> <p>$Q = A.B$</p> | A | B | Output Q |  |  |
| NOT | <p>In this gate the output is opposite to the input state, Mathematically,</p> <p>$Q=A$</p> | A | | Output Q |  |  |
| NOR | <p>The output is active high only if both the inputs are in active low state, Mathematically,</p> <p>$Q = (A+B)'$</p> | A | B | Output Q |  |  |
| NAND | <p>The output is active high only if any one of the input is in active low state, Mathematically,</p> <p>$Q = (A.B)'$</p> | A | B | Output Q |  |  |
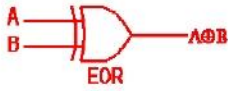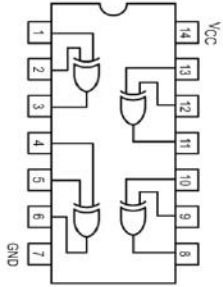
| | | | | | | |
|-----|--|---|---|----------|--|---|
| XOR | <p>The output is active high only if any one of the input is in active high state, Mathematically,</p> $Q = A.B' + B.A'$ | A | B | Output Q |  | <p>7486</p>  |
| | | 0 | 0 | 0 | | |
| | | 0 | 1 | 1 | | |
| | | 1 | 0 | 1 | | |
| | | 1 | 1 | 0 | | |

14 Pre lab Questions

1. What is truth table?
2. Which gates are called universal gates?
3. A basic 2-input logic circuit has a HIGH on one input and a LOW on the other input, and the output is HIGH. What type of logic circuit is it?
4. A logic circuit requires HIGH on all its inputs to make the output HIGH. What type of logic circuit is it?
5. Develop the truth table for a 3-input AND gate and also determine the total number of possible combinations for a 4-input AND gate.

VERILOG Program

a) AND Gate

| Structural Model | Data Flow Model | Behavioural Model |
|--|--|---|
| <pre>module andstr(x,y,z); input x,y; output z; and g1(z,x,y); endmodule</pre> | <pre>module anddf(x,y,z); input x,y; output z; assign z=(x&y); endmodule</pre> | <pre>module andbeh(x,y,z); input x,y; output z; reg z; always @(x,y) z=x&y; endmodule</pre> |

b) NAND Gate

| Structural Model | Data Flow Model | BehaviouralModel |
|---|--|--|
| modulenanandstr(x,y,z); inputx,y; output z; nand g1(z,x,y); endmodule | modulenanddf(x,y,z); inputx,y; output z; assign z= !(x&y); endmodule | module nandbeh(x,y,z); input x,y; output z; reg z; always @(x,y) z=!(x&y); endmodule |

c) OR Gate

| Structural Model | Data Flow Model | BehaviouralModel |
|--|---|---|
| module orstr(x,y,z); inputx,y; output z; or g1(z,x,y); endmodule | module ordf(x,y,z); inputx,y; output z; assign z=(x y); endmodule | module orbeh(x,y,z); input x,y; output z; reg z; always @(x,y) z=x y; endmodule |

d) NOR Gate

| Structural Model | Data Flow Model | BehaviouralModel |
|---|---|--|
| modulenorstr(x,y,z); inputx,y; output z; nor g1(z,x,y); endmodule | modulenordf(x,y,z); inputx,y; output z; assign z= !(x y); endmodule | Modulenorbeh(x,y,z); input x,y; output z; reg z; always @(x,y) z=!(x y); endmodule |

e) XOR Gate

| Structural Model | Data Flow Model | BehaviouralModel |
|---|---|---|
| <pre>module xorstr(x,y,z); inputx,y; output z; xor g1(z,x,y); endmodule</pre> | <pre>module xordf(x,y,z); inputx,y; output z; assign z=(x^y); endmodule</pre> | <pre>module xorbeh(x,y,z); input x,y; output z; reg z; always @(x,y) z=x^y; endmodule</pre> |

f) XNOR Gate

| Structural Model | Data Flow Model | BehaviouralModel |
|--|---|---|
| <pre>modulexnorstr(x,y,z); inputx,y; output z; xnor g1(z,x,y); endmodule</pre> | <pre>modulexnordf(x,y,z); inputx,y; output z; assign z= !(x^y); endmodule</pre> | <pre>module xnorbeh(x,y,z); input x,y; output z; reg z; always @(x,y) z=!(x^y); endmodule</pre> |

g) NOT Gate

| Structural Model | Data Flow Model | BehaviouralModel |
|--|--|--|
| <pre>module notstr(x,z); input x; output z; not g1(z,x); endmodule</pre> | <pre>module notdf(x,z); input x; output z; assign z= !x; endmodule</pre> | <pre>module notbeh(x,z); input x; output z; reg z; always @(x) z=!x; endmodule</pre> |

Out put waveforms

AND Gate:



RESULT

Thus the logic gates were implemented using XILINX .

EXP:

Design of Binary Adders

2.1 Introduction

The purpose of this experiment is to introduce the design of simple combinational circuits, in this case half adders, half subtractors, full adders and full subtractors.

2.2 Software tools Requirement

Equipments:

Computer with Modelsim Software

Specifications:

HP Computer P4 Processor - 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Softwares: Modelsim - 5.7c, Xilinx - 6.1i.

Algorithm

STEP 1: Open ModelSim XE II / Starter 5.7C

STEP 2: File -> Change directory -> D:\<register number>

STEP 3: File -> New Library -> ok

STEP 4: File -> New Source -> Verilog

STEP 5: Type the program

STEP 6: File -> Save -> <filename.v>

STEP 7: Compile the program

STEP 8: Simulate -> expand work -> select file -> ok

STEP 9: View -> Signals


STEP 10: Select values -> Edit -> Force -> input values

STEP 11: Add -> Wave -> Selected signals -> Run


STEP 12: Change input values and run again

2.3 Logic Diagram


Half adder

 


Full adder

 

Halfsubtractor

 

 

Full subtractor

24 Pre lab Questions

1. What is meant by combinational circuits?
2. Write the sum and carry expression for half and full adder.
3. Write the difference and borrow expression for half and full subtractor.
4. What is signal? How it is declared?
5. Design a one bit adder.

VERILOG Program

HALF ADDER:

| Structural model | Dataflow model | Behavioural model |
|---|--|---|
| <pre> module halfaddstr(sum, carry, a, b); output sum, carry; input a, b; xor(sum, a, b); and(carry, a, b); endmodule </pre> | <pre> module halfadddf(sum, carry, a, b); output sum, carry; input a, b; assign sum = a ^ b; assign carry = a & b; endmodule </pre> | <pre> module halfaddbeh(sum, carry, a, b); output sum, carry; input a, b; reg sum, carry; always @(a, b); sum = a ^ b; carry = a & b; endmodule </pre> |

FULL ADDER:

| Structural model | Dataflow model | Behaviouralmodel |
|---|--|--|
| <pre> module fulladdstr(sum,carry,a,b,c); outputsum,carry; inputa,b,c; xor g1(sum,a,b,c); and g2(x,a,b); and g3(y,b,c); and g4(z,c,a); or g5(carry,x,z,y); endmodule </pre> | <pre> modulefulladddf(sum,carry,a,b,c); outputsum,carry; inputa,b,c; assign sum = a ^ b^c; assign carry=(a&b) (b&c) (c&a); endmodule </pre> | <pre> modulefulladdbeh(sum,carry,a,b,c); outputsum,carry; inputa,b,c; regsum,carry; always @ (a,b,c) sum = a ^ b^c; carry=(a&b) (b&c) (c&a); endmodule </pre> |

HALF SUBTRACTOR:

| Structural model | Dataflow Model | BehaviouralModel |
|--|--|---|
| <pre> modulehalfsubtstr(diff,borrow,a,b); outputdiff,borrow; inputa,b; xor(diff,a,b); and(borrow,~a,b); endmodule </pre> | <pre> modulehalfsubtdf(diff,borrow,a,b); outputdiff,borrow; inputa,b; assign diff = a ^ b; assign borrow=(~a&b); endmodule </pre> | <pre> modulehalfsubtbeh(diff,borrow,a,b); outputdiff,borrow; inputa,b; regdiff,borrow; always @(a,b) diff = a ^ b; borrow=(~a&b); endmodule </pre> |

FULL SUBTRACTOR:

| Structural model | Dataflow Model | BehaviouralModel |
|--|---|---|
| <pre> module fullsubstr(diff,borrow,a,b,c); outputdiff,borrow; inputa,b,c; wire a0,q,r,s,t; not(a0,a); xor(x,a,b); xor(diff,x,c); and(y,a0,b); and(z,~x,c); or(borrow,y,z); endmodule </pre> | <pre> modulefullsubtdf(diff,borrow,a,b,c); outputdiff,borrow; inputa,b,c; assign diff = a^b^c; assign borrow=(~a&b) (~(a^b)&c); endmodule </pre> | <pre> modulefullsubtbeh(diff,borrow,a,b,c); outputdiff,borrow; inputa,b,c; outputdiff,borrow; always@(a,b,) diff = a^b^c; borrow=(~a&b) (~(a^b)&c); endmodule </pre> |

Output waveforms:


Half Adder:




Half subtractor:




Full adder Dataflow modeling:

 

Full adder structural modeling:

 

Full Subtractor Dataflow modeling:

 

RESULT

Thus the Half-adder, Full adder, Four bit adder were implemented using Xilinx.

EXP: Design of Ripple carry, Carry select and Carry save Adders

3.1 Introduction

The purpose of this experiment is to introduce the design of Ripple carry, Carry select and Carry save Adders

3.2 Software tools Requirement

Equipments:

Computer with Modelsim Software

Specifications:

HP Computer P4 Processor - 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Softwares: Modelsim - 5.7c, Xilinx - 6.1i.

Algorithm

STEP 1: Open ModelSim XE II / Starter 5.7C

STEP 2: File -> Change directory -> D:\<register number>

STEP 3: File -> New Library -> ok

STEP 4: File -> New Source -> Verilog

STEP 5: Type the program

STEP 6: File -> Save -> <filename.v>

STEP 7: Compile the program

STEP 8: Simulate -> expand work -> select file -> ok

STEP 9: View -> Signals

STEP 10: Select values -> Edit -> Force -> input values

STEP 11: Add -> Wave -> Selected signals -> Run

STEP 12: Change input values and run again

3.3 Ripple carry adder


VHDL Program

8-bit Ripple Carry Adder

| Structural code for RCA | Test bench for RCA |
|---|---|
| <pre>module rippe_adder(X, Y, S, Co); input [3:0] X, Y; output [3:0] S; output Co; wire w1, w2, w3; fulladder u1(X[0], Y[0], 1'b0, S[0], w1); fulladder u2(X[1], Y[1], w1, S[1], w2); fulladder u3(X[2], Y[2], w2, S[2], w3); fulladder u4(X[3], Y[3], w3, S[3], Co); endmodule module fulladder(X, Y, Ci, S, Co); input X, Y, Ci; output S, Co; wire w1,w2,w3; xor G1(w1, X, Y); xor G2(S, w1, Ci); and G3(w2, w1, Ci); and G4(w3, X, Y); or G5(Co, w2, w3); endmodule</pre> | <pre>ENTITY Tb_Ripple_Adder IS END Tb_Ripple_Adder; ARCHITECTURE behavior OF Tb_Ripple_Adder IS -- Component Declaration for the Unit Under Test (UUT) COMPONENT Ripple_Adder PORT(A : IN std_logic_vector(3 downto 0); B : IN std_logic_vector(3 downto 0); Cin : IN std_logic; S : OUT std_logic_vector(3 downto 0); Cout : OUT std_logic); END COMPONENT; --Inputs signal A : std_logic_vector(3 downto 0) := (others => '0'); signal B : std_logic_vector(3 downto 0) := (others => '0'); signal Cin : std_logic := '0'; --Outputs signal S : std_logic_vector(3 downto 0); signal Cout : std_logic; BEGIN -- Instantiate the Unit Under Test (UUT) uut: Ripple_Adder PORT MAP (A => A, B => B, Cin => Cin, S => S, Cout => Cout); -- Stimulus process stim_proc: process begin -- hold reset state for 100 ns. wait for 100 ns; A <= "0110"; B <= "1100"; wait for 100 ns;</pre> |


| | |
|--|---|
| | <pre> A <= "1111"; B <= "1100"; wait for 100 ns; A <= "0110"; B <= "0111"; wait for 100 ns; A <= "0110"; B <= "1110"; wait for 100 ns; A <= "1111"; B <= "1111"; wait; end process; END; </pre> |
|--|---|

Output Waveform

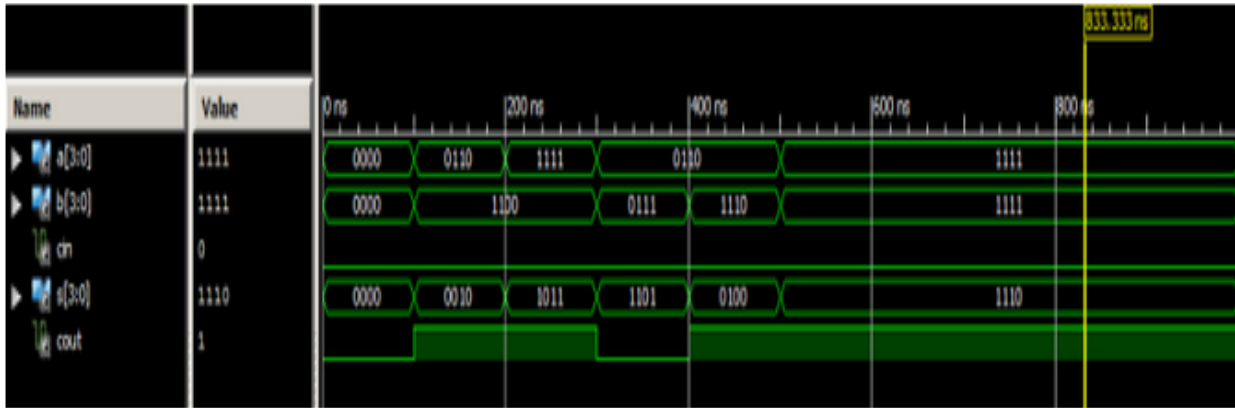

3.4 Carry select adder

Logic diagram

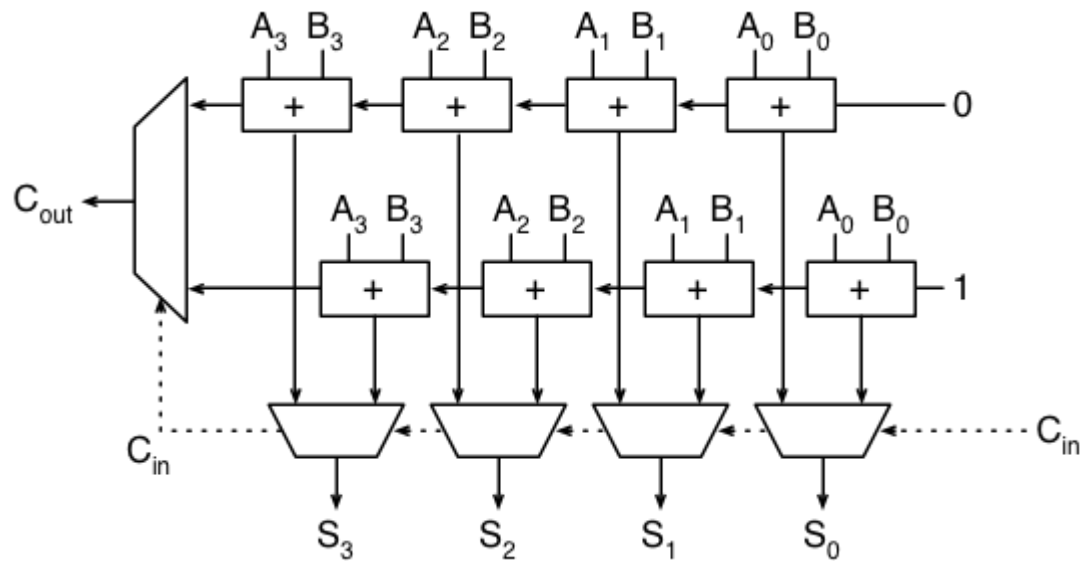

Verilog program

| Structural code for CSA | Structural code for CSA |
|--|---|
| <pre> Module carry_select (a,b,s,cin,cout); Input [3:0]a,b; Input cin; Output cout; Output [3:0]s; Wire [3:0]s; Wire Cout; Wire s1,c1,s2,c2,s3,c3,s4,c4,s11,c11,s22,c22,s33,c33,s44,c44; fa x1(a[0],b[0],0,s1,c1); fa x2(a[1],b[1],c1,s2,c2); fa x3(a[2],b[2],c2,s2,c2); fa x4(a[3],b[3],c3,s3,c3); fa x5(a[0],b[0],1,s11,c11); fa x6(a[1],b[1],c11,s22,c22); fa x7(a[2],b[2],c22,s33,c33); fa x8(a[3],b[3],c33,s44,c44); mux x9(s1,s11,cin,s[0]); mux x10(s2,s22,cin,s[1]); mux x11(s3,s33,cin,s[2]); mux x12(s4,s44,cin,s[3]); mux x12(c4,c44,cin,cout); endmodule </pre> | <pre> ENTITY Tb_carry_select_adder IS END Tb_carry_select_adder; ARCHITECTURE behavior OF Tb_carry_select_adder IS -- Component Declaration for the Unit Under Test (UUT) COMPONENT carry_select_adder PORT (X : IN std_logic_vector(3 downto 0); Y : IN std_logic_vector(3 downto 0); CARRY_IN : IN std_logic; SUM : OUT std_logic_vector(3 downto 0); CARRY_OUT : OUT std_logic); END COMPONENT; --Inputs signal X : std_logic_vector(3 downto 0) := (others=> '0'); signal Y : std_logic_vector(3 downto 0) := (others=> '0'); signal CARRY_IN : std_logic := '0'; --Outputs signal SUM : std_logic_vector(3 downto 0); signal CARRY_OUT : std_logic; BEGIN </pre> |

```

-- Instantiate the Unit Under
Test (UUT)
 uut: carry_select_adder PORT MAP
 (
  X => X,
  Y => Y,
  CARRY_IN => CARRY_IN,
  SUM => SUM,
  CARRY_OUT => CARRY_OUT
 );

-- Stimulus process
 stim_proc: process
 begin
  -- hold reset state for 100 ns.
  wait for 100 ns;
  X <= "1011";
  Y <= "1111";


  wait for 100 ns;
  X <= "0001";
  Y <= "1010";

  wait for 100 ns;
  X <= "0111";
  Y <= "1111";
  wait;
 end process;

END;


```

Output waveform of CSA

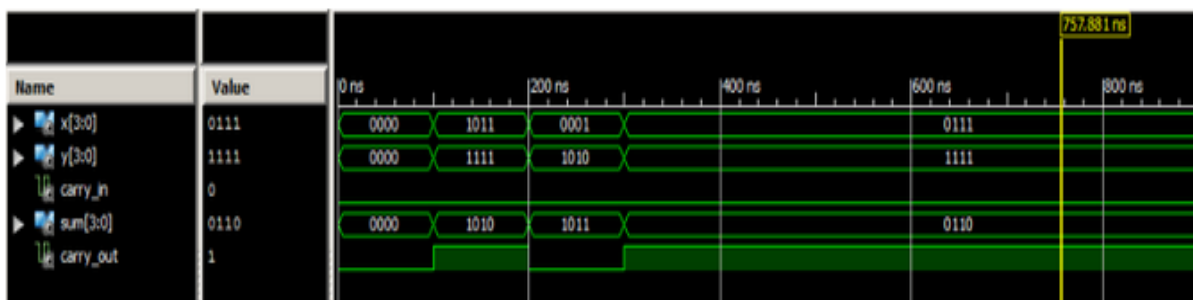

3.5 Carry save adder

Logic diagram

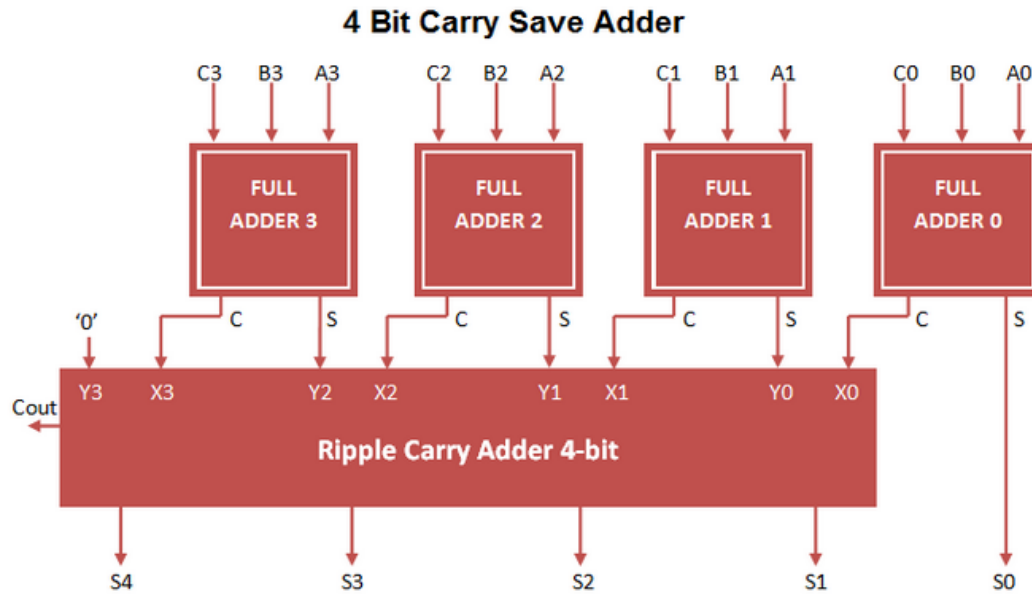


VHDL Program

| Structural code for CSA | Test bench for CSA |
|--|---|
| <pre> entity carry_save_adder is Port (A : in STD_LOGIC_VECTOR (3 downto 0); B : in STD_LOGIC_VECTOR (3 downto 0); C : in STD_LOGIC_VECTOR (3 downto 0); S : OUT STD_LOGIC_VECTOR (4 downto 0); Cout : OUT STD_LOGIC); end carry_save_adder; architecture Behavioral of carry_save_adder is component full_adder_vhdl_code Port (A : in STD_LOGIC; B : in STD_LOGIC; Cin : in STD_LOGIC; S : out STD_LOGIC; Cout : out STD_LOGIC); end component; -- Intermediate signal signal X,Y: STD_LOGIC_VECTOR(3 downto 0); signal C1,C2,C3: STD_LOGIC; begin -- Carry save adder block FA1: full_adder_vhdl_code PORT MAP(A(0),B(0),C(0),S(0),X(0)); FA2: full_adder_vhdl_code PORT MAP(A(1),B(1),C(1),Y(0),X(1)); FA3: full_adder_vhdl_code PORT MAP(A(2),B(2),C(2),Y(1),X(2)); FA4: full_adder_vhdl_code PORT MAP(A(3),B(3),C(3),Y(2),X(3)); -- Ripple carry adder block FA5: full_adder_vhdl_code PORT MAP(X(0),Y(0),'0',S(1),C1); FA6: full_adder_vhdl_code PORT MAP(X(1),Y(1),C1,S(2),C2); FA7: full_adder_vhdl_code PORT MAP(X(2),Y(2),C2,S(3),C3); FA8: full_adder_vhdl_code PORT MAP(X(3),'0',C3,S(4),Cout); end Behavioral; </pre> | <pre> ENTITY Tb_carry_save IS END Tb_carry_save; ARCHITECTURE behavior OF Tb_carry_save IS -- Component Declaration for the Unit Under Test (UUT) COMPONENT carry_save_adder PORT(A : IN std_logic_vector(3 downto 0); B : IN std_logic_vector(3 downto 0); C : IN std_logic_vector(3 downto 0); S : OUT std_logic_vector(4 downto 0); Cout : OUT std_logic); END COMPONENT; --Inputs signal A : std_logic_vector(3 downto 0) := (others=> '0'); signal B : std_logic_vector(3 downto 0) := (others=> '0'); signal C : std_logic_vector(3 downto 0) := (others=> '0'); --Outputs signal S : std_logic_vector(4 downto 0); signal Cout : std_logic; BEGIN -- Instantiate the Unit Under Test (UUT) uut: carry_save_adder PORT MAP (A => A, B => B, C => C, S => S, Cout => Cout); -- Stimulus process stim_proc: process begin -- hold reset state for 100 ns. wait for 100 ns; A <= "1100"; B <= "1101"; C <= "1110"; wait for 100 ns; A <= "1111"; B <= "1000"; C <= "1001"; </pre> |

| | |
|--|--|
| | <pre> wait for 100 ns; A <= "1110"; B <= "0101"; C <= "0111"; wait; end process; END;</pre> |
|--|--|

Output waveform

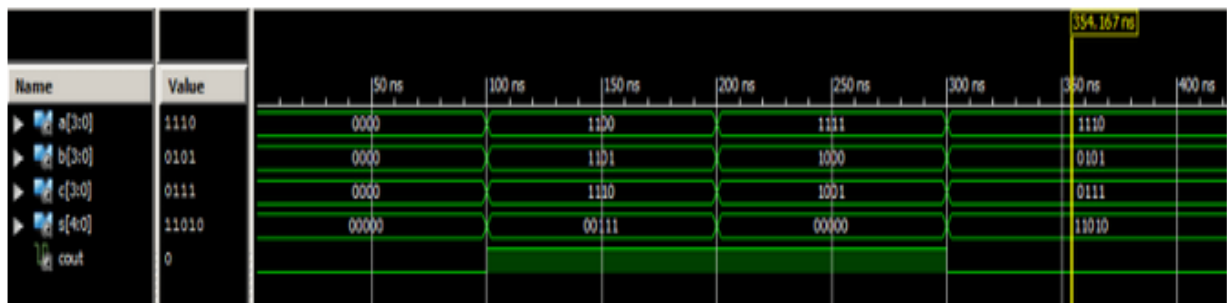

RESULT

Thus the Ripple carry, Carry select and Carry save Adders were implemented using XILINX .

EXP: Design of Multiplexers and Demultiplexers

4.1 Introduction

The purpose of this experiment is to write and simulate a VERILOG program for Multiplexers and Demultiplexers.

4.2 Software tools Requirement:

Equipments:

Computer with Modelsim Software

Specifications:

HP Computer P4 Processor - 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Softwares: Modelsim - 5.7c, Xilinx - 6.1i.

Algorithm

STEP 1: Open ModelSim XE II / Starter 5.7C

STEP 2: File -> Change directory -> D:\<register number>

STEP 3: File -> New Library -> ok

STEP 4: File -> New Source -> Verilog

STEP 5: Type the program

STEP 6: File -> Save -><filename.v>

STEP 7: Compile the program

STEP 8: Simulate -> expand work -> select file -> ok


STEP 9: View -> Signals

STEP 10: Select values -> Edit -> Force -> input values

STEP 11: Add -> Wave -> Selected signals -> Run

STEP 12: Change input values and run again


43 **Logic Diagram**

 

| s_1 | s_0 | Y |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

Function Table

4:1 Multiplexer Block diagram

 


| S_1 | S_0 | F_0 | F_1 | F_2 | F_3 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | D | 0 | 0 | 0 |
| 0 | 1 | 0 | D | 0 | 0 |
| 1 | 0 | 0 | 0 | D | 0 |
| 1 | 1 | 0 | 0 | 0 | D |


1:4 Demux Symbol

Function Table

Logic Diagram

 

2:1 Multiplexer

 

4:1 Multiplexer

44 Pre lab Questions

1. Define mux and demux. Write
2. their applications.
3. What is the relationship b/w input lines and select lines.
4. Design 4:1 mux and 1:4 demux.
5. Write brief notes on case statement.

VERILOG Program


Multiplexers 2:1 MUX

| Structural Model | Dataflow Model | BehaviouralModel |
|---|--|---|
| <pre>module mux21str(i0,i1,s,y); input i0,i1,s; output y; wire net1,net2,net3; not g1(net1,s); and g2(net2,i1,s); and g3(net3,i0,net1); or g4(y,net3,net2); endmodule</pre> | <pre>module mux21df(i0,i1,s,y); input i0,i1,s; output y; assign y =(i0&(~s)) (i1&s); endmodule</pre> | <pre>module mux21beh(i0,i1,s,y); input i0,i1,s; output y; reg y; always@(i0,i1) begin if(s==0) y=i1; if(s==1)y=i0; end endmodule</pre> |

4:1 MUX

| Structural Model | Dataflow Model | BehaviouralModel |
|--|--|---|
| <pre>module mux41str(i0,i1,i2,i3,s0,s1,y); input i0,i1,i2,i3,s0,s1; wire a,b,c,d; output y; and g1(a,i0,s0,s1); and g2(b,i1,(~s0),s1); and g3(c,i2,s0,(~s1)); and g4(d,i3,(~s0),(~s1)); or(y,a,b,c,d); endmodule</pre> | <pre>module mux41df(i0,i1,i2,i3,s0,s1,y); input i0,i1,i2,i3,s0,s1; output y; assign y=((i0&(~(s0))&(~(s1))) (i1&(~(s0))&s1) (i2&s0&(~(s1))) (i3&s0&s1); endmodule</pre> | <pre>module mux41beh(in,s,y); output y ; input [3:0] in ; input [1:0] s ; reg y; always @ (in,s) begin if (s[0]==0&s[1]==0) y = in[3]; else if (s[0]==0&s[1]==1) y = in[2]; else if (s[0]==1&s[1]==0) y = in[1]; else y = in[0]; end endmodule</pre> |

Logic Diagram

 


8:1 Multiplexer

VERILOG Program


8:1 MUX

| Structural Model | Dataflow Model | Behavioural Model |
|--|--|--|
| <pre>module mux81str(i0,i1,i2,i3,i4,i5,i6,i7,s0,s1,s2,y); input i0,i1,i2,i3,i4,i5,i6,i7,s0,s1,s2; wire a,b,c,d,e,f,g,h; output y; and g1(a,i7,s0,s1,s2); and g2(b,i6,(~s0),s1,s2); and g3(c,i5,s0,(~s1),s2); and g4(d,i4,(~s0),(~s1),s2); and g5(e,i3,s0,s1,(~s2)); and g6(f,i2,(~s0),s1,(~s2)); and g7(g,i1,s0,(~s1),(s2)); and g8(h,i0,(~s0),(~s1),(~s2)); or(y,a,b,c,d,e,f,g,h); endmodule</pre> | <pre>module mux81df(y,i,s) ; output y; input [7:0] i; input [2:0] s; wire sel; assign sel=(s[2]*4) (s[1]*2) (s[0]); assign y=i[sel]; endmodule</pre> | <pre>module mux81beh(s,i0,i1,i2,i3,i4,i5,i6,i7,y); input [2:0] s; input i0,i1,i2,i3,i4,i5,i6,i7; reg y; always@(i0,i1,i2,i3,i4,i5,i6,i7,s) begin gin case(s) begin 3'd0:MUX_OUT=i0; 3'd1:MUX_OUT=i1; 3'd2:MUX_OUT=i2; 3'd3:MUX_OUT=i3; 3'd4:MUX_OUT=i4; 3'd5:MUX_OUT=i5; 3'd6:MUX_OUT=i6; 3'd7:MUX_OUT=i7; endcase end endmodule</pre> |

Logic Diagram

 

1:4 Demultiplexer

 

1:8 Demultiplexer

VERILOG Program

1:4 DEMUX

| Structural Model | Dataflow Model | BehaviouralModel |
|--|--|---|
| <pre>module demux14str(in,d0,d1,d2,d3,s0,s1); in output d0,d1,d2,d3; input in,s0,s1; and g1(d0,in,s0,s1); and g2(d1,in,(~s0),s1); and g3(d2,in,s0,(~s1)); and g4(d3,in,(~s0),(~s1)); endmodule</pre> | <pre>module demux14df(d0,d1,d2,d3,s0,s1); output d0,d1,d2,3; input in,s0,s1; assign s0 = in & (~s0) & (~s1); assign d1= in & (~s0) & s1; assign d2= in & s0 & (~s1); assign d3= in & s0 & s1; endmodule</pre> | <pre>module demux14beh(din,sel,dout); output [3:0] dout ; reg [3:0] dout ; input din ; wire din ; input [1:0] sel ; wire [1:0] sel ; always @ (din or sel) begin case (sel) 0 : dout = {din,3'b000}; 1 : dout = {1'b0,din,2'b00}; 2 : dout = {2'b00,din,1'b0}; default : dout = {3'b000,din}; endcase end endmodule</pre> |

1:8 DEMUX

| Structural Model | Dataflow Model | BehaviouralModel |
|---|--|--|
| <pre> module demux18str(in,s0,s1,s2,d0,d1,d2 ,d3,d4,d5,d6,d7); input in,s0,s1,s2; output d0,d1,d2,d3,d4,d5,d6,d7; and g1(d0,in,s0,s1,s2); and g2(d1,in,(~s0),s1,s2); and g3(d2,in,s0,(~s1),s2); and g4(d3,in,(~s0),(~s1),s2); and g5(d4,in,s0,s1,(~s2)); and g6(d5,in,(~s0),s1,(~s2)); and g7(d6,in,s0,(~s1),(~s2)); and g8(d7,in,(~s0),(~s1),(~s2)); endmodule </pre> | <pre> module demux18df(in,s0,s1,s2,i0,d1,d2,d3,d4,d5 ,d6,d7); input in,s0,s1,s2; output d0,d1,d2,d3,d4,d5,d6,d7; assign d0 = in & s0 & s1 & s2; assign d1 = in & (~s0) & s1 & s2; assign d2 = in & s0 & (~s1) & s2; assign d3 = in & (~s0) & (~s1) & s2; assign d4 = in & s0 & s1 & (~s2); assign d5 = in & (~s0) & s1 & (~s2); assign d6 = in & s0 & (~s1) & (~s2); assign d7 = in & (~s0) & (~s1) & (~s2); endmodule </pre> | <pre> module demux18beh(i, sel, y); input i; input [2:0] sel; output [7 :0] y ; reg [7:0] y; always@(i,sel) begin y=8'd0; case(sel) 3'd0:y[0]=i; 3'd1:y[1]=i; 3'd2:y[2]=i; 3'd3:y[3]=i; 3'd4:y[4]=i; 3'd5:y[5]=i; 3'd6:y[6]=i; default:y[7]=i; endcase end endmodule </pre> |

Output Wave forms:


2 X 1 MUX:




4 X 1 MUX DATAFLOW MODELING




4 X 1 MUX STRUCTURAL MODELING

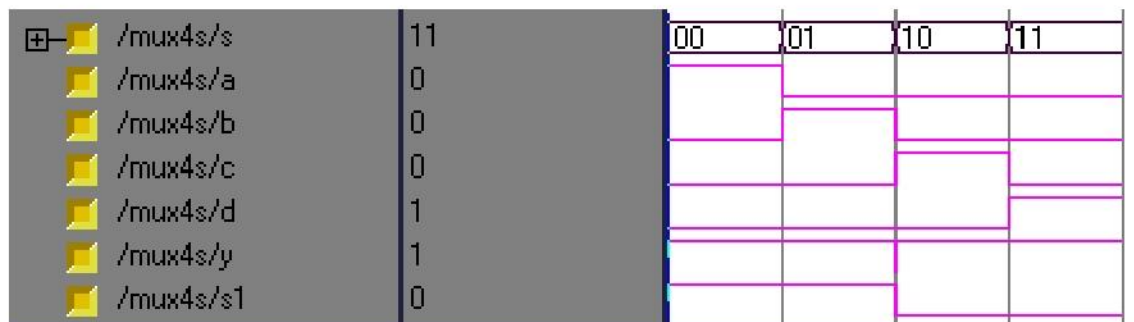

MUX 8:1 Using 4:1 & 2:1

 

1 TO 4 DEMUX BEHAVIOURAL MODELING

 

8 bit multiplier

VHDL Program


Structural code for multiplier

```
module multipliermod(a, b, out);  
input [4:0] a;  
input [4:0] b;  
output [9:0] out;  
assign out=(a*b);  
endmodule
```

TEST BENCH

```
module multiplierr_b;  
reg [4:0] a;  
reg [4:0] b;  
wire [9:0] out;  
multipliermod uut (.a(a),.b(b),.out(out) );  
initial begin  
#10 a=4'b1000;b=4'b0010;  
#10 a=4'b0010;b=4'b0010;  
#10 a=4'b0100;b=4'b0100;  
#10 a=4'b1000;b=4'b0001;  
#10$stop;  
end  
endmodule
```

Output waveform

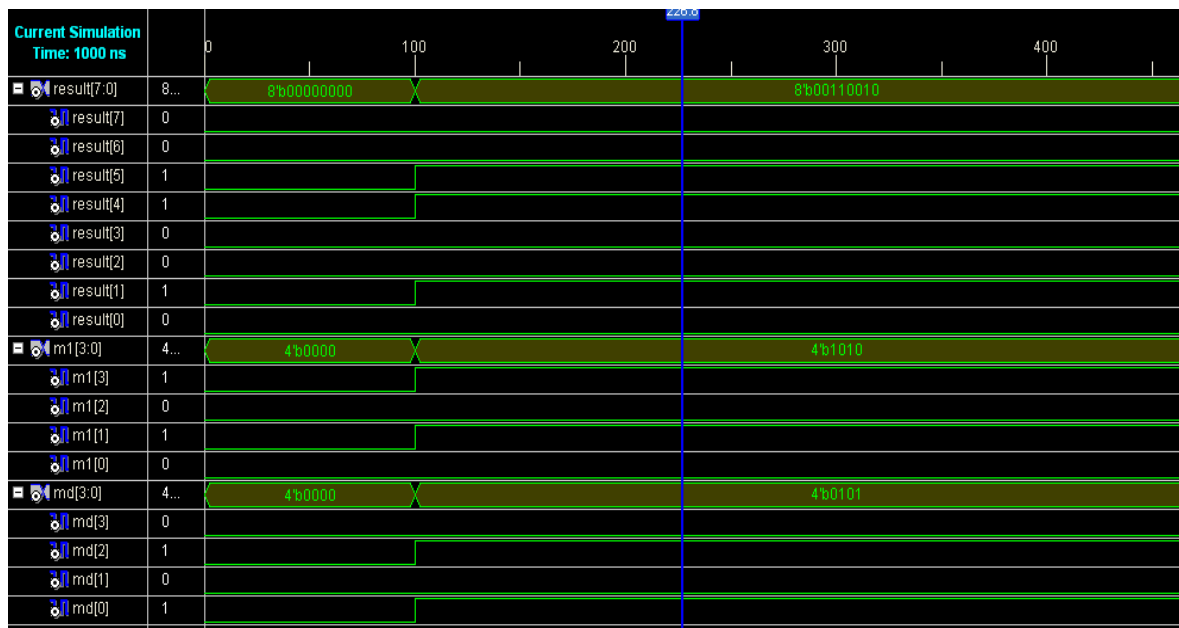

RESULT

Thus the multiplexers, demultiplexers and 8 bit Multiplier were simulated using Xilinx.

EXP 5:

Design of Flip Flops

5.1 Introduction

The purpose of this experiment is to introduce you to the basics of flip-flops. In this lab, you will test the behavior of several flip-flops and you will connect several logic gates together to create simple sequential circuits.

5.2 Software tools Requirement

Equipments:

Computer with Modelsim Software

Specifications:

HP Computer P4 Processor - 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Softwares: Modelsim - 5.7c, Xilinx - 6.1i.

Algorithm

STEP 1: Open ModelSim XE II / Starter 5.7C

STEP 2: File -> Change directory -> D:\<register number>

STEP 3: File -> New Library -> ok

STEP 4: File -> New Source -> Verilog

STEP 5: Type the program

STEP 6: File -> Save -> <filename.v>

STEP 7: Compile the program

STEP 8: Simulate -> expand work -> select file -> ok

STEP 9: View -> Signals

STEP 10: Select values -> Edit -> Force -> input values

STEP 11: Add -> Wave -> Selected signals -> Run

STEP 12: Change input values and run again

53 Flip-Flops Logic diagram and their properties

Flip-flops are synchronous bitable devices. The term synchronous means the output changes state only when the clock input is triggered. That is, changes in the output occur in synchronization with the clock.

A flip-flop circuit has two outputs, one for the normal value and one for the complement value of the stored bit. Since memory elements in sequential circuits are usually flip-flops, it is worth summarizing the behavior of various flip-flop types before proceeding further.

All flip-flops can be divided into four basic types: SR, JK, D and T. They differ in the number of inputs and in the response invoked by different value of input signals. The four types of flip-flops are defined in the Table 5.1. Each of these flip-flops can be uniquely described by its graphical symbol, its characteristic table, its characteristic equation or excitation table. All flip-flops have output signals Q and Q'.







| Flip-Flop Name | Flip-Flop Symbol | Characteristic Table | Characteristic Equation | Excitation Table | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
|----------------|---|--|-------------------------|------------------|---------|---|---|----|-----------------------------|--|---|---------|---|---|---|---|----|--|--|---|---------|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| SR |  | <table><tr><th>S</th><th>R</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td><td>Q</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>?</td></tr></table> | S | R | Q(next) | 0 | 0 | Q | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | ? | $Q(\text{next}) = S + R'Q$ $SR = 0$ | <table><tr><th>Q</th><th>Q(next)</th><th>S</th><th>R</th></tr><tr><td>0</td><td>0</td><td>0</td><td>X</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>X</td><td>0</td></tr></table> | Q | Q(next) | S | R | 0 | 0 | 0 | X | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | X | 0 |
| S | R | Q(next) | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | Q | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | ? | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| Q | Q(next) | S | R | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | X | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | X | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| JK |  | <table><tr><th>J</th><th>K</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td><td>Q</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td></td><td>1</td><td>Q'</td></tr></table> | J | K | Q(next) | 0 | 0 | Q | 0 | 1 | 0 | 1 | 0 | 1 | | 1 | Q' | $Q(\text{next}) = JQ' + K'Q$ | <table><tr><th>Q</th><th>Q(next)</th><th>J</th><th>K</th></tr><tr><td>0</td><td>0</td><td>0</td><td>X</td></tr><tr><td>0</td><td>1</td><td>1</td><td>X</td></tr><tr><td>1</td><td>0</td><td>X</td><td>1</td></tr><tr><td>1</td><td>1</td><td>X</td><td>0</td></tr></table> | Q | Q(next) | J | K | 0 | 0 | 0 | X | 0 | 1 | 1 | X | 1 | 0 | X | 1 | 1 | 1 | X | 0 |
| J | K | Q(next) | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | Q | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | 1 | Q' | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| Q | Q(next) | J | K | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | X | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | X | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | X | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | X | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| D |  | <table><tr><th>D</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table> | D | Q(next) | 0 | 0 | 1 | 1 | $Q(\text{next}) = D$ | <table><tr><th>Q</th><th>Q(next)</th><th>D</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> | Q | Q(next) | D | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | | | | | | | | | | | | | | |
| D | Q(next) | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| Q | Q(next) | D | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| T |  | <table><tr><th>T</th><th>Q(next)</th></tr><tr><td>0</td><td>Q</td></tr><tr><td>1</td><td>Q'</td></tr></table> | T | Q(next) | 0 | Q | 1 | Q' | $Q(\text{next}) = TQ' + TQ$ | <table><tr><th>Q</th><th>Q(next)</th><th>T</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> | Q | Q(next) | T | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | | | | | | | | | | | | | | |
| T | Q(next) | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | Q | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | Q' | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| Q | Q(next) | T | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |


Table 5.3 Flip-flops and their properties




D- Flip Flop

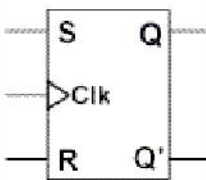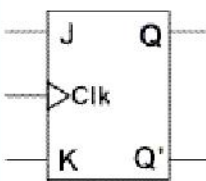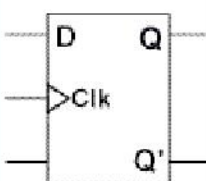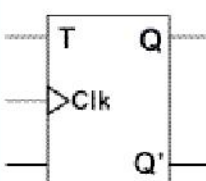  

JK Flip Flop

 

T Flip Flop

 

S Flip Flop

5.4 Pre-lab Questions

1. Describe the main difference between a gated S-R latch and an edge-triggered S-R flip-flop.
2. How does a JK flip-flop differ from an SR flip-flop in its basic operation?
3. Describe the basic difference between pulse-triggered and edge-triggered flip-flops.
4. What is use of characteristic and excitation table?
5. What are synchronous and asynchronous circuits?
6. How many flip flops due you require storing the data 1101?

Verilog prohram

S-R Flip Flop

| Behavioral Modelling | Structural Modelling | Dataflow Modelling |
|---|--|--|
| <pre>modulesr_df(s, r, q, q_n); input s, r; output q, q_n; assignq_n = ~(s q); assign q = ~(r q_n); endmodule</pre> | <pre>module sr_st(s,r,q,q_n); input s, r; output q, q_n; or g1(q_n,~s,~q); or g2(q,~r,~q_n); endmodule</pre> | <pre>module sr_beh(s,r,q,q_n); input s, r; output q, q_n; regq, q_n; always@(s,r) begin q,n = ~(s q); assign q = ~(r q_n); endmodule</pre> |

T Flip Flop

| Behavioral Modelling | Structural Modelling | Dataflow Modelling |
|---|--|--|
| <pre>module t_beh(q,q1,t,c); output q,q1; inputt,c; reg q,q1; initial begin q=1'b1; q1=1'b0; end always @ (c) begin if(c) begin</pre> | <pre>module t_st(q,q1,t,c); output q,q1; input t,c; wire w1,w2; assign w1=t&c&q; assign w2=t&c&q1; assign q=~(w1 q1); assign q1=~(w2 q); endmodule</pre> | <pre>module t_df(q,q1,t,c); output q,q1; input t,c; and g1(w1,t,c,q); and g2(w2,t,c,q1); nor g3(q,w1,q1); nor g4(q1,w2,q); endmodule</pre> |

| | | |
|---|--|--|
| <pre> if (t==1'b0) begin q=q; q1=q1; end else begin q=~q; q1=~q1; end end end end module </pre> | | |
|---|--|--|

D flip flop

| Behavioral Modelling | Structural Modelling | Dataflow Modelling |
|--|--|--|
| <pre> Module dff_async_reset(data, clk, reset ,q); input data, clk, reset ; output q; reg q; always @ (posedgeclk or negedge reset) if (~reset) begin q <= 1'b0; end else begin q <= data; end </pre> | <pre> module dff_df(d,c,q,q1); input d,c; output q,q1; assign w1=d&c; assign w2=~d&c; q=~(w1 q1); q1=~(w2 q); endmodule </pre> | <pre> module dff_df(d,c,q,q1); input d,c; output q,q1; and g1(w1,d,c); and g2(w2,~d,c); nor g3(q,w1,q1); nor g4(q1,w2,q); endmodule </pre> |

JK flip flop

| Behavioral Modelling | Structural Modelling | Dataflow Modelling |
|---|--|---|
| <pre> module jk(q,q1,j,k,c); output q,q1; input j,k,c; reg q,q1; initial begin q=1'b0; q1=1'b1; end always @ (posedge c) begin case({j,k}) {1'b0,1'b0}:begin q=q; q1=q1; end {1'b0,1'b1}: begin q=1'b0; q1=1'b1; end {1'b1,1'b0}:begin q=1'b1; q1=1'b0; end {1'b1,1'b1}: begin q=~q; q1=~q1; end endcase </pre> | <pre> module jkflip_df (j,k,q,qn); input j,k,q; output qn; wire w1,w2; assign w1=~q; assign w2=~k; assign qn=(j & w1 w2 & q); endmodule </pre> | <pre> module jkflip_st(j,k,q,qn); input j,k,q; output qn; and g1(w1,j,~q); and g2(w2,~k,q); or g3(qn,w1,w2); endmodule </pre> |

| | | |
|-----|--|--|
| end | | |
|-----|--|--|

Output Waveforms

D flip flop



T flip flop



RESULT

Thus the VHDL code for flip-flop was implemented and simulated using Xilinx.

EXP : Design of Counters

6.1 Introduction

The purpose of this experiment is to introduce the design of Synchronous Counters, asynchronous, ring, johnson up/down Counter.

6.2 Software tools Requirement

Equipments:

Computer with Modelsim Software

Specifications:

HP Computer P4 Processor - 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Softwares: Modelsim - 5.7c, Xilinx - 6.1i.

Algorithm

STEP 1: Open ModelSim XE II / Starter 5.7C

STEP 2: File -> Change directory -> D:\<register number>

STEP 3: File -> New Library -> ok

STEP 4: File -> New Source -> Verilog

STEP 5: Type the program

STEP 6: File -> Save -><filename.v>

STEP 7: Compile the program

STEP 8: Simulate -> expand work -> select file -> ok


STEP 9: View -> Signals

STEP 10: Select values -> Edit -> Force -> input values

STEP 11: Add -> Wave -> Selected signals -> Run

STEP 12: Change input values and run again

63 Logic Diagram

 

Verilog program

Up down counter


Verilog code

```
module updown(out,clk,reset,updown);
output [3:0]out;
input clk,reset,updown;
reg [3:0]out;
always @(posedge clk)
if(reset) begin
out<= 4'b0;
end else if(updown) begin
out<=out+1;
end else if(!updown) begin
out<=out-1;
end
endmodule
```

Asynchronous counter & Synchronous Counters


| VHDL code | VHDL code |
|---|--|
| <pre>entity counter_8 is port(clk,en,rst:in std_logic; count:out std_logic_vector(7 downto 0)); end counter_8; architecture beh of counter_8 is signal cnt:std_logic_vector(7 downto 0); begin process(clk,en,rst) begin if(rst='0')then cnt<=(others=>'0'); elsif(clk'event and clk='1')then if(en='1')then cnt<=cnt+'1';end if;end if; end process;count<=cnt; end beh;</pre> | <pre>entity counter is port(C, S : in std_logic; Q : out std_logic_vector(3 downto 0)); end counter; architecture archi of counter is signal tmp: std_logic_vector(3 downto 0); begin process (C) begin if (C'event and C='1') then if (S='1') then tmp <= "1111"; else tmp <= tmp - 1; end if; end if; end process; Q <= tmp; end archi;</pre> |

Output Waveform

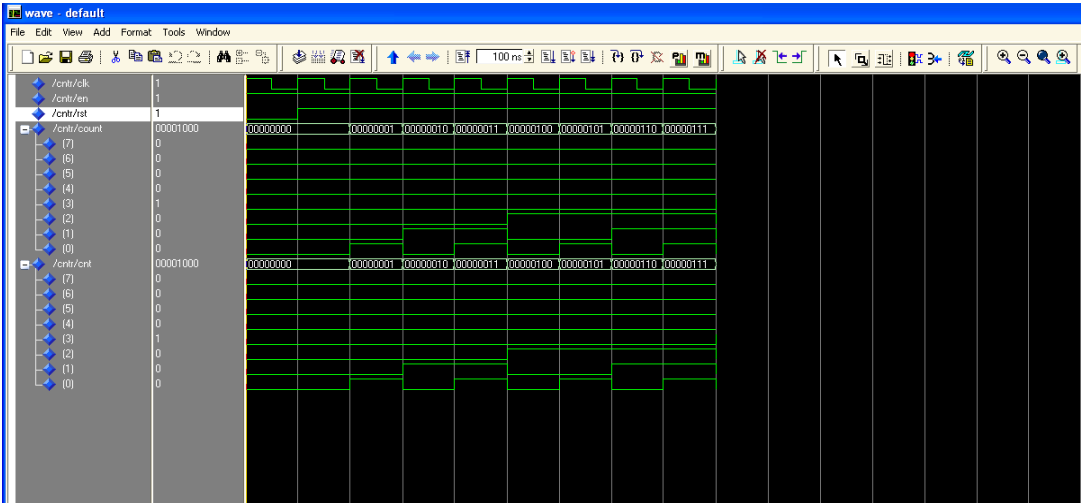


Ring counter & Johnson counter

Logic diagram

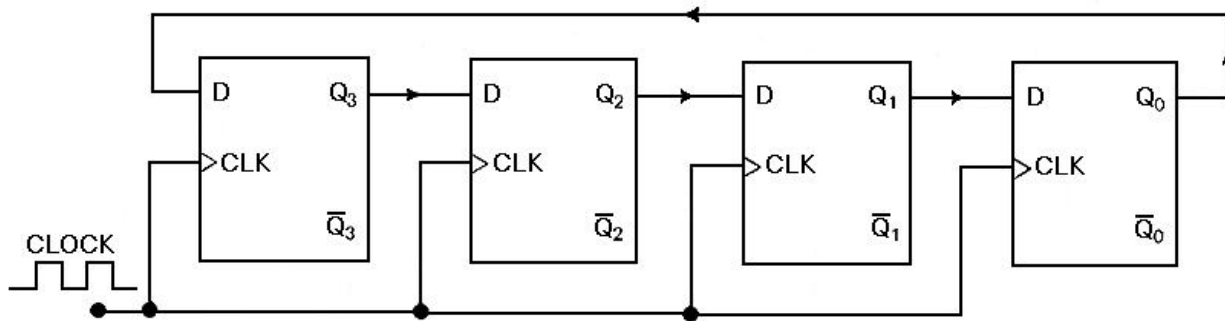

Ring counter

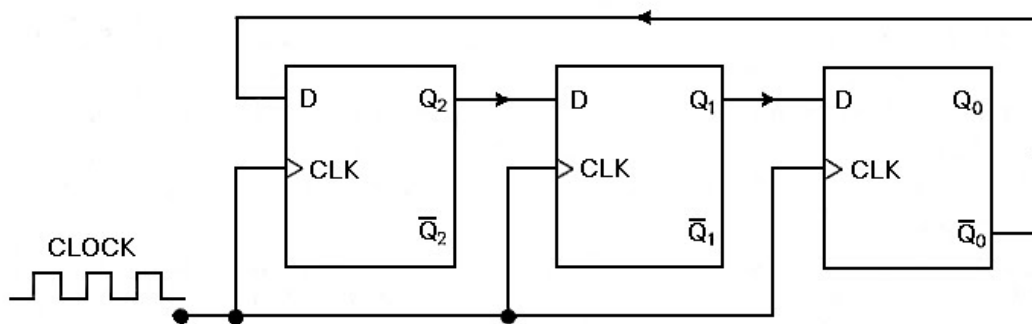


Johnson counter

VHDL program


| Ring counter | Johnson counter |
|--|--|
| <pre>entity ring_counter is '0'); begin DAT_O <= temp; process(CLK_I) begin if(rising_edge(CLK_I)) then if (RST_I = '1') then temp <= (0=> '1', others => '0');</pre> | <pre>entity johnson_counter is port (DAT_O : out unsigned(3 downto 0); RST_I : in std_logic; CLK_I : in std_logic); end johnson_counter; architecture Behavioral of johnson_counter is signal temp : unsigned(3 downto 0):=(others => '0');</pre> |

| | |
|--|--|
| <pre> else temp(1) <= temp(0); temp(2) <= temp(1); temp(3) <= temp(2); temp(0) <= temp(3); end if; end if; end process; end Behavioral; </pre> | <pre> begin DAT_O <= temp; process(CLK_I) begin if(rising_edge(CLK_I)) then if (RST_I = '1') then temp <= (others => '0'); else temp(1) <= temp(0); temp(2) <= temp(1); temp(3) <= temp(2); temp(0) <= not temp(3); end if; end if; end process; end Behavioral; </pre> |
|--|--|

Output waveform

 

Ring counter

 

Johnson counter

RESULT

Thus the Counter VHDL code were implemented and simulated by using Xilinx project navigator

EXP: Design of State machines

1.1 Introduction

The purpose of this experiment is to simulate the behavior of Moore and Mealy model

1.2 Software tools Requirement

Equipments:

Computer with Modelsim Software

Specifications:

HP Computer P4 Processor - 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Softwares: Modelsim - 5.7c, Xilinx - 8.1i.

Algorithm

STEP 1: Open ModelSim XE II / Starter 5.7C

STEP 2: File -> Change directory -> D:\<register number>

STEP 3: File -> New Library -> ok

STEP 4: File -> New Source -> Verilog

STEP 5: Type the program

STEP 6: File -> Save -><filename.v>

STEP 7: Compile the program

STEP 8: Simulate -> expand work -> select file -> ok


STEP 9: View -> Signals

STEP 10: Select values -> Edit -> Force -> input values


STEP 11: Add -> Wave -> Selected signals -> Run

STEP 12: Change input values and run again

Mealy model

 

Moore model

 

State Transition Diagram

Program

| VHDL Moore model | Verilog Mealy model |
|--|---|
| <pre> entity mealy is port (clk : in std_logic; reset : in std_logic; input : in std_logic; output : out std_logic); end mealy; architecture behavioral of mealy is type state_type is (s0,s1,s2,s3); --type of state </pre> | <pre> module seq_dect (input clk, data_in, reset, output reg data_out); // Declare state register reg [2:0]state; // Declare states parameter S0 = 0, S1 = 1, S2 = 2, S3 = 3, S4 = 4; </pre> |

```

machine.
signal current_s,next_s: state_type; --current
and next state declaration.

begin

process (clk,reset)
begin
if (reset='1') then
current_s <= s0; --default state on reset.
elsif (rising_edge(clk)) then
current_s <= next_s; --state change.
end if;
end process;
--state machine process.
process (current_s,input)
begin
case current_s is
when s0 => --when current state is "s0"
if(input ='0') then
output <= '0';
next_s <= s1;
else
output <= '1';
next_s <= s2;
end if;
when s1 => --when current state is
"s1"
if(input ='0') then
output <= '0';
next_s <= s3;
else
output <= '0';
next_s <= s1;
end if;

when s2 => --when current state is "s2"
if(input ='0') then
output <= '1';
next_s <= s2;
else
output <= '0';
next_s <= s3;
end if;

when s3 => --when current state is "s3"
if(input ='0') then
output <= '1';
next_s <= s3;

```

```

// Determine the next state
always @ (posedge clk or posedge reset)
begin
if (reset)
state <= S0;
else
case (state)
S0:
if (data_in)
state <= S1;
else
state <= S0;
S1:
if (data_in)
state <= S1;
else
state <= S2;
S2:
if (data_in)
state <= S3;
else
state <= S2;
S3:
if (data_in)
state <= S4;
else
state <= S2;
S4:
if (data_in)
state <= S1;
else
state <= S2;
endcase // case (state)
end // always @ (posedge clk or posedge
reset)
// Output depends only on the state
always @ (state) begin
case (state)
S0:
data_out = 1'b0;
S1:
data_out = 1'b1;
S2:
data_out = 1'b0;
S3:
data_out = 1'b1;
S4:
data_out = 1'b1;

```

```

else
  output <= '1';
  next_s <= s0;
end if;
end case;
end process;

end behavioral;

```

```


default:
  data_out = 1'b0;
endcase // case (state)
end // always @ (state)

endmodule // moore_mac


```

Output waveform

Mealy model

 

Moore model

 

RESULT

Thus the Moore and Mealy state machines code were implemented and simulated by using Xilinx project navigator

EXP: Design of CMOS inverter

8.1 Introduction

To perform the functional verification of the CMOS Inverter through schematic entry

8.2 Software tools Requirement

S-Edit using cadance Tool

HP Computer P4 Processor - 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Algorithm


STEP 1: Draw the schematic of CMOS Inverter using S-edit.

STEP 2: Perform Transient Analysis of the CMOS Inverter.


STEP 3: Obtain the output waveform from W-edit

STEP 4: Obtain the spice code using T-edit.


Circuit diagram of CMOS inverter

 

CIRCUIT USING TANNER

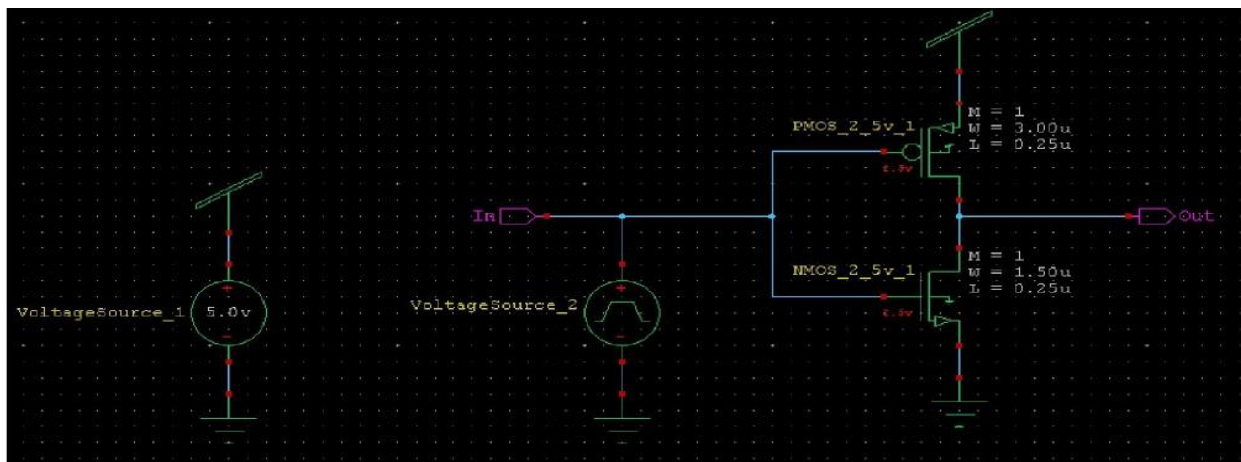

SIMULATED WAVEFORM:

 

RESULT

Thus the functional verification of the CMOS Inverter through schematic entry and the output also verified successfully.

EXP: Design of Differential Amplifier

8.1 Introduction

To calculate the gain, bandwidth and CMRR of a differential amplifier through schematic entry.

8.2 Software tools Requirement

S-Edit using cadance Tool

HP Computer P4 Processor - 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Algorithm

STEP 1: Draw the schematic of differential amplifier using S-edit and generate the symbol.



STEP 2: Draw the schematic of differential amplifier circuit using the generated symbol.



STEP 3: Perform AC Analysis of the differential amplifier.

STEP 4: Obtain the frequency response from W-edit.

STEP 5: Obtain the spice code using T-edit.

SCHEMATIC DIAGRAM:

 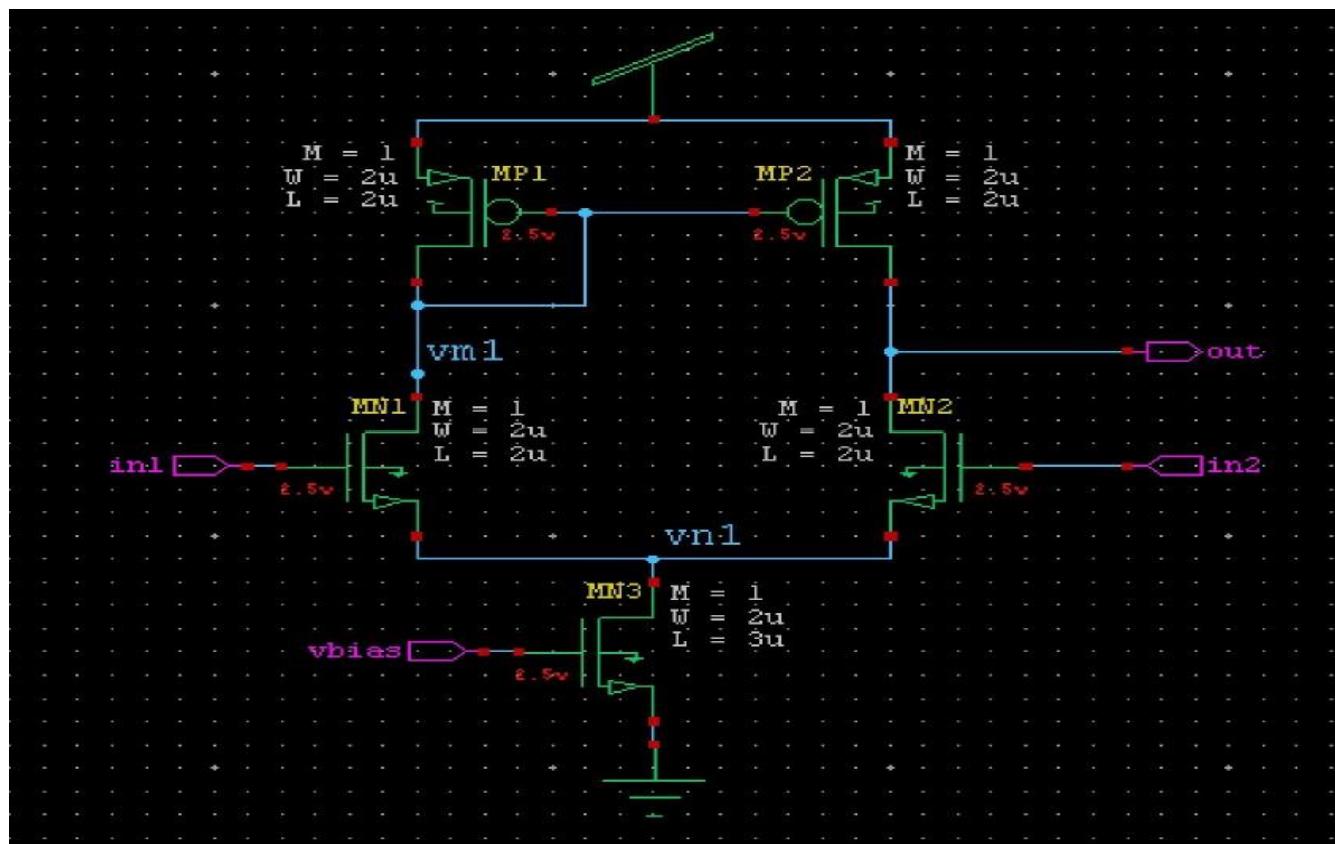

 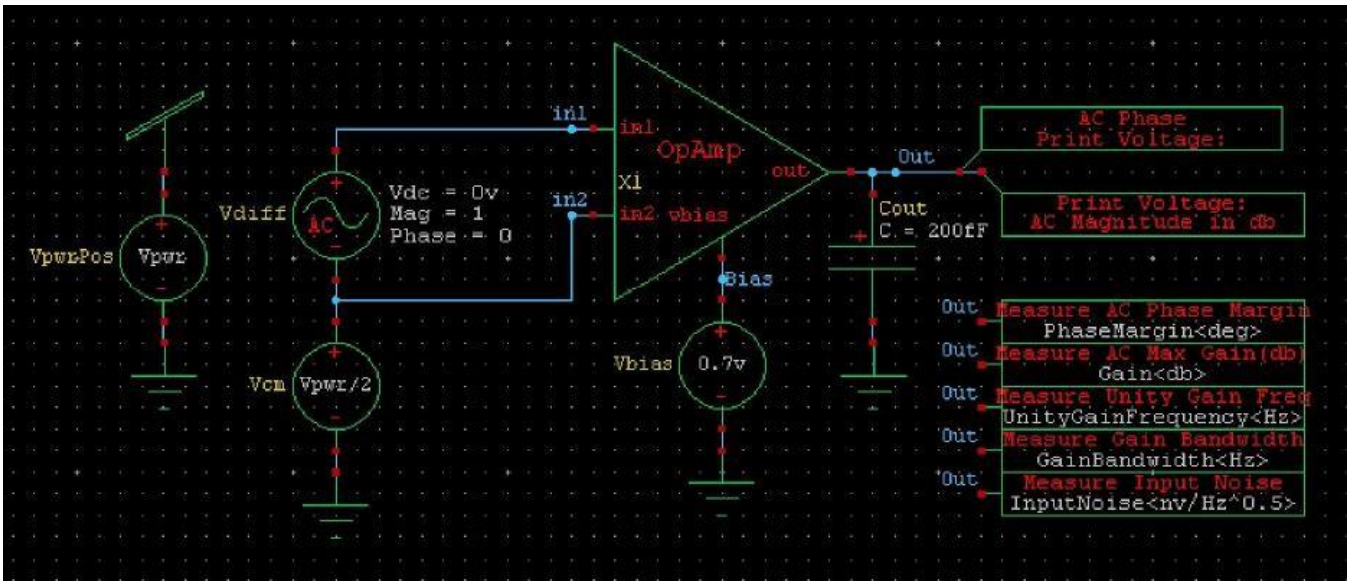

RESULT

Thus the functional verification of the **Differential Amplifier** through schematic entry and the output also verified successfully.

EXP: CMOS LOGIC GATES

Aim:

To Synthesize CMOS logic gates using Tanner

Description:

- **Logic NAND** $f(V_1, V_2) = (V_1 V_2)' = V_1' + V_2'$:


The pull-down function is $f' = V_1 V_2$, the pull-up function is $(V_1 V_2)' = V_1' + V_2'$. The output function $V_{out} = f(V_1, V_2) = V_1' + V_2' = (V_1 V_2)'$ is the same as the pull-up function, a negation of AND, or NAND.

- **Logic NOR** $f(V_1 + V_2) = (V_1 + V_2)' = V_1' V_2'$:

The pull-down function is $f' = V_1 + V_2$, the pull-up function is $(V_1 + V_2)' = V_1' V_2'$. The output is the same as the pull-up function $V_{out} = (V_1 + V_2)'$, negation of OR, or NOR.

| | | AND | OR | NAND | NOR |
|-------|-------|-----------|-------------|--------------|----------------|
| V_1 | V_2 | $V_1 V_2$ | $V_1 + V_2$ | $(V_1 V_2)'$ | $(V_1 + V_2)'$ |
| 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 |

Diagram:

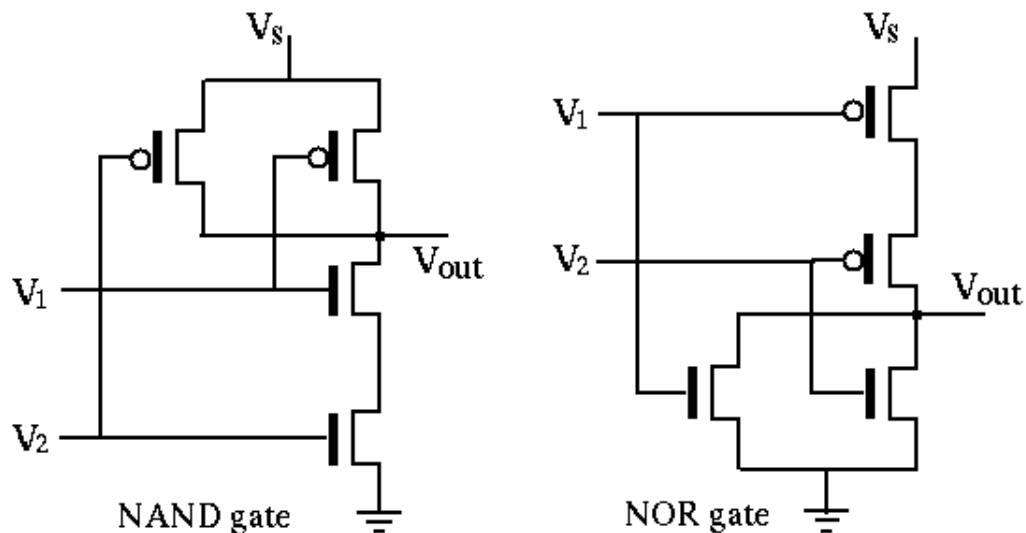

Result:

EXP:

DESIGN OF ALU

Aim:

To Design an ALU and simulate using Xilinx.

PROGRAM:

```
module alu(  
    input [7:0] A,B, // ALU 8-bit Inputs  
    input [3:0] ALU_Sel, // ALU Selection  
    output [7:0] ALU_Out, // ALU 8-bit Output  
    output CarryOut // Carry Out Flag  
);  
    reg [7:0] ALU_Result;  
    wire [8:0] tmp;  
    assign ALU_Out = ALU_Result; // ALU out  
    assign tmp = {1'b0,A} + {1'b0,B};  
    assign CarryOut = tmp[8]; // Carryout flag  
    always @(*)  
    begin  
        case (ALU_Sel)  
            4'b0000: // Addition  
                ALU_Result = A + B ;  
            4'b0001: // Subtraction  
                ALU_Result = A - B ;  
            4'b0010: // Multiplication  
                ALU_Result = A * B;  
            4'b0011: // Division  
                ALU_Result = A/B;  
            4'b0100: // Logical shift left  
                ALU_Result = A<<1;  
            4'b0101: // Logical shift right  
                ALU_Result = A>>1;  
            4'b0110: // Rotate left  
                ALU_Result = {A[6:0],A[7]};  
            4'b0111: // Rotate right
```

```

        ALU_Result = {A[0],A[7:1]};
4'b1000: // Logical and
        ALU_Result = A & B;
4'b1001: // Logical or
        ALU_Result = A | B;
4'b1010: // Logical xor
        ALU_Result = A ^ B;
4'b1011: // Logical nor
        ALU_Result = ~(A | B);
4'b1100: // Logical nand
        ALU_Result = ~(A & B);
4'b1101: // Logical xnor
        ALU_Result = ~(A ^ B);
4'b1110: // Greater comparison
        ALU_Result = (A>B)?8'd1:8'd0 ;
4'b1111: // Equal comparison
        ALU_Result = (A==B)?8'd1:8'd0 ;
default: ALU_Result = A + B ;
endcase
end

endmodule

```

RESULT:

EXP: DESIGN OF UNIVERSAL SHIFT REGISTER

Aim:

To Design a universal shift register and simulate using Xilinx.

DESCRIPTION:

Universal shift register is capable of converting input data to **parallel** or **serial** which also does shifting of data bidirectional, unidirectional (SISO , SIPO , PISO , PIPO) and also parallel load this is called as **Universal shift register** .

Shift register are used as: Data storage device , Delay element , communication lines , digital electronic devices (Temporary data storage , data transfer , data manipulation , counters), etc .

Function table

| Mode Control | | Register operation |
|--------------|----|--------------------|
| S1 | S0 | |
| 0 | 0 | No change |
| 0 | 1 | Shift left |
| 1 | 0 | Shift right |
| 1 | 1 | Parallel load |

Block diagram of universal shift register(USR) :

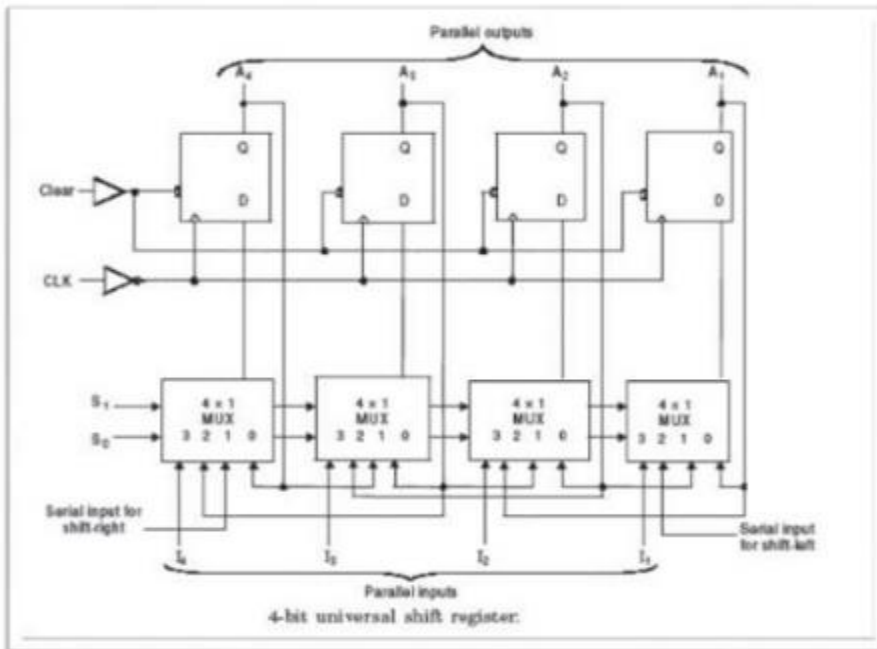


Figure block diagram of USR.

PROGRAM :

```

module Universal_shift_reg (data_out, msb_out, lsb_out, data_in,
msb_in, lasb_in, s1, s0, clk, rst);

output [3:0] data_out;          // Hold
output  msb_out, lsb_out;      // Serial shift from msb
input  [3:0] data_in;          // Serial shift from lsb
input  msb_in, lasb_in;        // Parallel load
input  s1, s0, clk, rst;
reg    data_out;

assign msb_out= data_out[3];
assign lsb_out= data_out[0];

always @ (posedge clk)

```

```
begin
  if (rst) data_out<=0;
  else case ({s1, s0})
    0 : data_out <= data_out;
    1 : data_out <= {msb_in, data_out[3:1]};
    2 : data_out <= {data_out[2:0], lsb_in};
    3 : data_out <= data_in;
  endcase
end
endmodule
```

RESULT:

EXP: DESIGN OF MEMORY**Aim:**

To Design a memory and simulate using Xilinx.

DESCRIPTION:**Verilog Code for 16x4 Memory**

| Sr. No. | Name of the Pin | Direction | Width | Description |
|---------|-----------------|-----------|-------|--|
| 1 | Address | Input | 4 | Input address |
| 2 | Ip | input | 4 | Input data to memory |
| 3 | Rd_wr | Input | 1 | Control signal 1=read from memory 0=write in to memory |
| 4 | Clk | Input | 1 | Clock input |
| 5 | op | Output | 4 | Output read from memory |

PROGRAM:

```
module memory_16x4 (op, ip, rd_wr, clk, address);
    output reg [3:0] op;
    input [3:0] ip;
    input [3:0] address;
    input rd_wr, clk;
    reg [3:0] memory[0:15];

    always @(posedge clk)
        begin
            if (rd_wr)
                op=memory[address];
            else
                begin
                    memory[address]=ip;
                end
            end
        end
endmodule // memory_16x4
```


RESULT:

EXP:**DESIGN OF CMOS INVERTING AMPLIFIER****Aim:**


To Design and simulate a CMOS inverting amplifier.

DESCRIPTION:

A CMOS inverter can also be viewed as a high gain amplifier. It consists of one PMOS device, M_1 and one NMOS device M_2 . Generally the CMOS fabrication process is designed such that the threshold voltage, V_{TH} , of the NMOS and PMOS devices are roughly equal i.e. complementary. The designer of the inverter then adjusts the width to length ratio, W/L , of the NMOS and PMOS devices such that their respective transconductance is also equal.

 

CMOS Inverting amplifier

 **RESULT:**


EXP: DESIGN OF COMMON SOURCE, COMMON GATE AND COMMON DRAIN AMPLIFIER

Aim:


To Design and simulate a CS,CG and CD amplifier.

DESCRIPTION:



COMMON SOURCE AMPLIFIER:

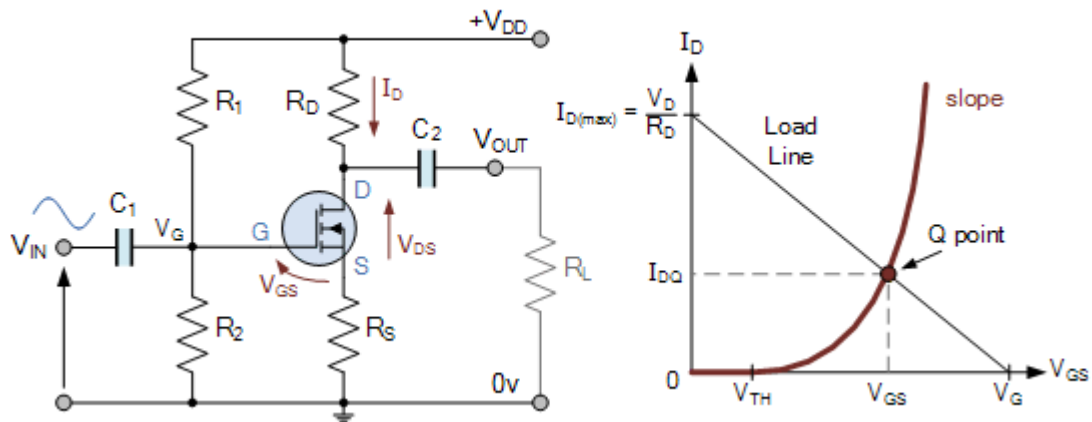

COMMON DRAIN AMPLIFIER:

 

COMMON GATE AMPLIFIER

  

RESULT: